Electronics/Circuit Design

Detector Circuits

Rudolf F. Graf

Why waste time paging through huge encyclopedias when you can choose the topic you need and select any of the specialized circuits already sorted by application? *Detector Circuits* provides fast, easy access to more than 300 ready-to-use circuits in their original form. Circuits include:

- Air-Flow Detectors
- Electrostatic Detectors
- Gas/Smoke/Vapor Detectors
- Lie Detectors
- Liquid Detectors
- Metal Detectors
- Peak Detectors
- Phase Detectors
- Power-Failure Detectors
- Radar Detectors
- Radiation Detectors
- Voice/Sound Detectors

Each schematic is accompanied by a brief explanation of how the circuit works, and the original source is given in a section at the back of the book, making it easy to obtain further information.

Other titles in this series:

Amplifier Circuits
Converter and Filter Circuits
Measuring Circuits
Oscillator Circuits

Rudolf F. Graf is a full-time technical author whose name is familiar to electronics professionals and hobbyists alike. His many books offer a practical and enjoyable approach to often-complex material. Mr. Graf is a graduate electronics engineer, and received his MBA at New York University. He is a senior member of the IEEE, a licensed amateur radio operator, and a holder of a first-class radiotelephone operator's license. He currently lives in New York.

Newnes
An imprint of Butterworth–Heinemann

Contents

	Introduction	*vii*
1	Air-Flow Detectors	*1*
2	Bug Detector	*4*
3	Decoders	*6*
4	Demodulators	*18*
5	Descramblers	*22*
6	Electrostatic Detector	*26*
7	Flow Detectors	*28*
8	Gas/Smoke/Vapor Detectors	*32*
9	Hall-Effect Detectors	*47*
10	Ice-Formation Detectors	*54*
11	Level Detectors	*57*
12	Lie Detector	*61*
13	Liquid Detectors	*63*

14	Metal Detectors	***76***
15	Miscellaneous Detectors	***81***
16	Moisture Detectors	***89***
17	Null Detector	***94***
18	Optical Detectors	***96***
19	Overspeed Detectors	***104***
20	Overvoltage/Current Detector	***109***
21	Peak Detectors	***115***
22	Phase Detectors	***129***
23	Power-Failure Detectors	***135***
24	Proximity Detectors	***139***
25	Pulse Detectors	***148***
26	Radar Detectors	***154***
27	Radiation Detectors	***157***
28	Rain Detectors	***166***
29	Stereo Balance Detectors	***169***
30	Telephone Detectors	***172***
31	Tilt/Level Detectors	***179***
32	Touch Detectors	***183***
33	Voice/Sound Detectors	***197***
34	Window Detectors	***202***
35	Zero-Crossing Detectors	***210***
	Sources	***214***
	Index	***221***